

Electrical Systems

Kirchhoff's laws to transfer functions, and the electrical-mechanical analogy.

Ogata, *Modern Control Engineering*, Ch. 3.

In this tutorial you will:

- model a series RLC circuit with KVL,
- see the force-voltage analogy with the mass-spring-damper, and
- model an op-amp PI controller circuit.

Step through with **Ctrl+Enter**, or render a report with **publish**.

Electrical circuits are modeled with Kirchhoff's voltage and current laws. Consider a series RLC circuit driven by source voltage $e_i(t)$, with output taken as the voltage across the capacitor $e_o(t)$. KVL around the loop, with loop current $i(t)$:

$$L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt = e_i$$

and since $e_o = \frac{1}{C} \int i dt$, we have $i = C\dot{e}_o$. Substituting:

$$LC\ddot{e}_o + RC\dot{e}_o + e_o = e_i$$

Contents

- Transfer Function of the RLC Circuit
- The Electrical-Mechanical Analogy
- Operational-Amplifier Circuit
- Try it yourself

Transfer Function of the RLC Circuit

Taking the Laplace transform with zero initial conditions:

$$(LCs^2 + RCs + 1)E_o(s) = E_i(s) \Rightarrow G(s) = \frac{E_o(s)}{E_i(s)} = \frac{1}{LCs^2 + RCs + 1}$$

With $L = 1 \text{ H}$, $R = 2 \Omega$, $C = 0.5 \text{ F}$:


```
L = 1; R = 2; C = 0.5;
G_rlc = tf(1,[L*C R*C 1])

figure
[es,ts] = step(G_rlc);
plot(ts, ones(size(ts)), 'k--', ts, es, 'b', 'LineWidth', 1.3)
legend('Input voltage step $e_i$ (before)', 'Capacitor voltage $e_o(t)$ (after)', ...
       'Interpreter', 'latex', 'FontSize', 11, 'Location', 'east')
title('Input vs. Output: Series RLC Circuit', 'Interpreter', 'latex', 'FontSize', 16)
ylabel('amplitude', 'Interpreter', 'latex', 'FontSize', 16)
set(get(gca, 'YLabel'), 'Rotation', 0)
xlabel('$t$', 'Interpreter', 'latex', 'FontSize', 20)

G_rlc =

      1
-----
0.5 s^2 + s + 1

Continuous-time transfer function.
```

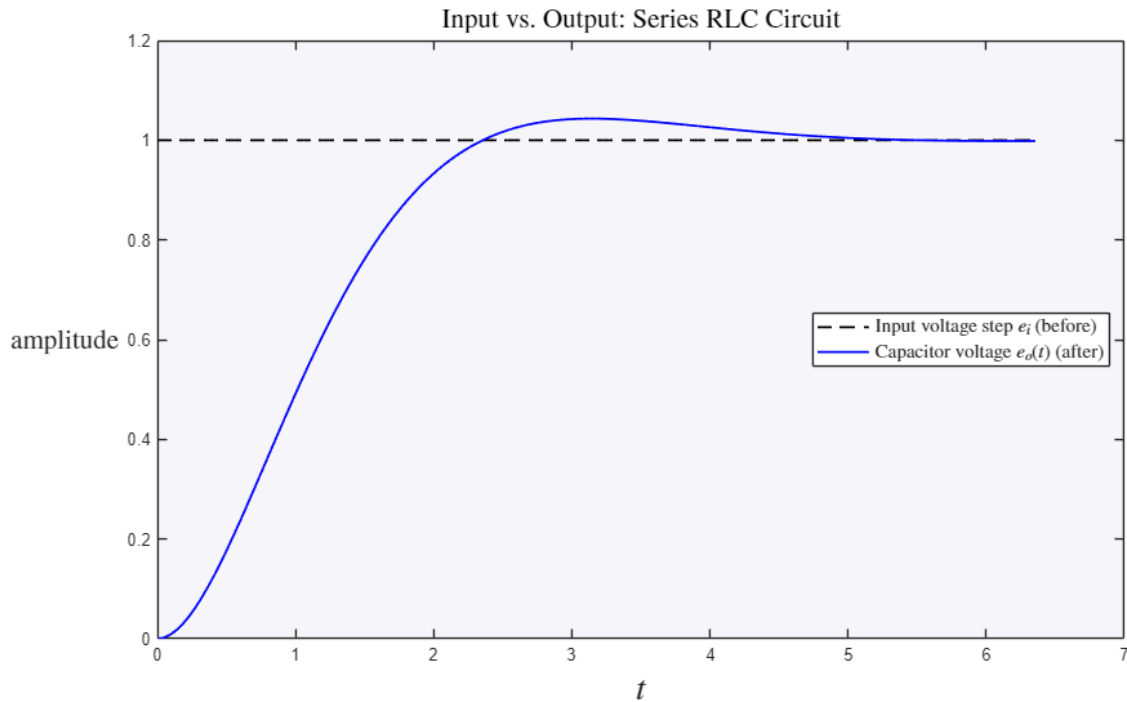

The Electrical-Mechanical Analogy

The RLC circuit equation is structurally identical to the mass-spring-damper equation $m\ddot{x} + b\dot{x} + kx = u$ from `MechanicalSystems.m`, under the force-voltage analogy:

Mechanical	Electrical
Force, u	Voltage, e
Mass, m	Inductance, L
Damping coeff., b	Resistance, R
Spring const., k	Elastance, $1/C$
Displacement, x	Charge, q
Velocity, dx/dt	Current, i

This analogy is why the same transfer-function machinery (and the same MATLAB code) applies to both physical domains.

Operational-Amplifier Circuit

A common building block is the inverting op-amp circuit with input impedance $Z_i(s)$ and feedback impedance $Z_f(s)$, giving

$$\frac{E_o(s)}{E_i(s)} = -\frac{Z_f(s)}{Z_i(s)}$$

For a PI-controller circuit, $Z_i = R_1$ (a resistor) and $Z_f = R_2 + \frac{1}{C_2 s}$ (a resistor and capacitor in series):

$$G(s) = -\frac{R_2 + \frac{1}{C_2 s}}{R_1} = -\frac{R_2 C_2 s + 1}{R_1 C_2 s}$$


```
R1 = 10e3; R2 = 20e3; C2 = 1e-6;
G_opamp = tf(-[R2*C2 1],[R1*C2 0])
```

```
figure
bode(G_opamp)
title('Op-Amp PI Circuit Frequency Response','Interpreter','latex','FontSize',20)
```

G_opamp =

$$\frac{-0.02 \text{ s} - 1}{0.01 \text{ s}}$$

Continuous-time transfer function.

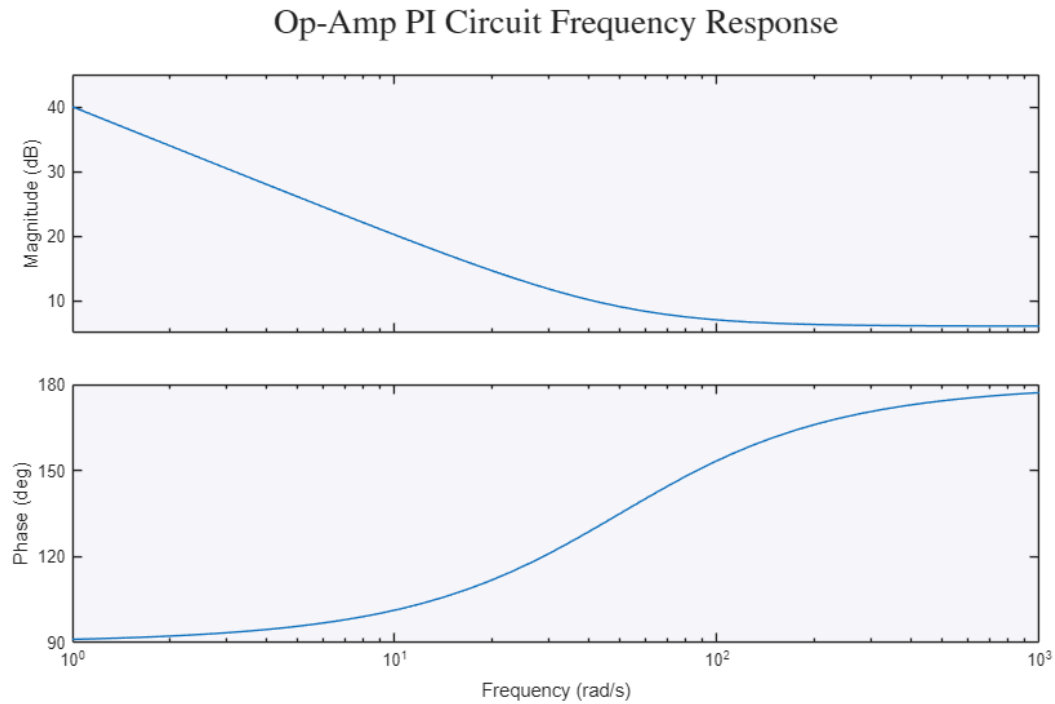

Try it yourself

- Shrink R toward 0 and notice the RLC response become more oscillatory (less damping) – the electrical twin of a light mechanical damper.
- Check the analogy: build the mass-spring-damper with $m=L$, $b=R$, $k=1/C$ and confirm its poles match the circuit.